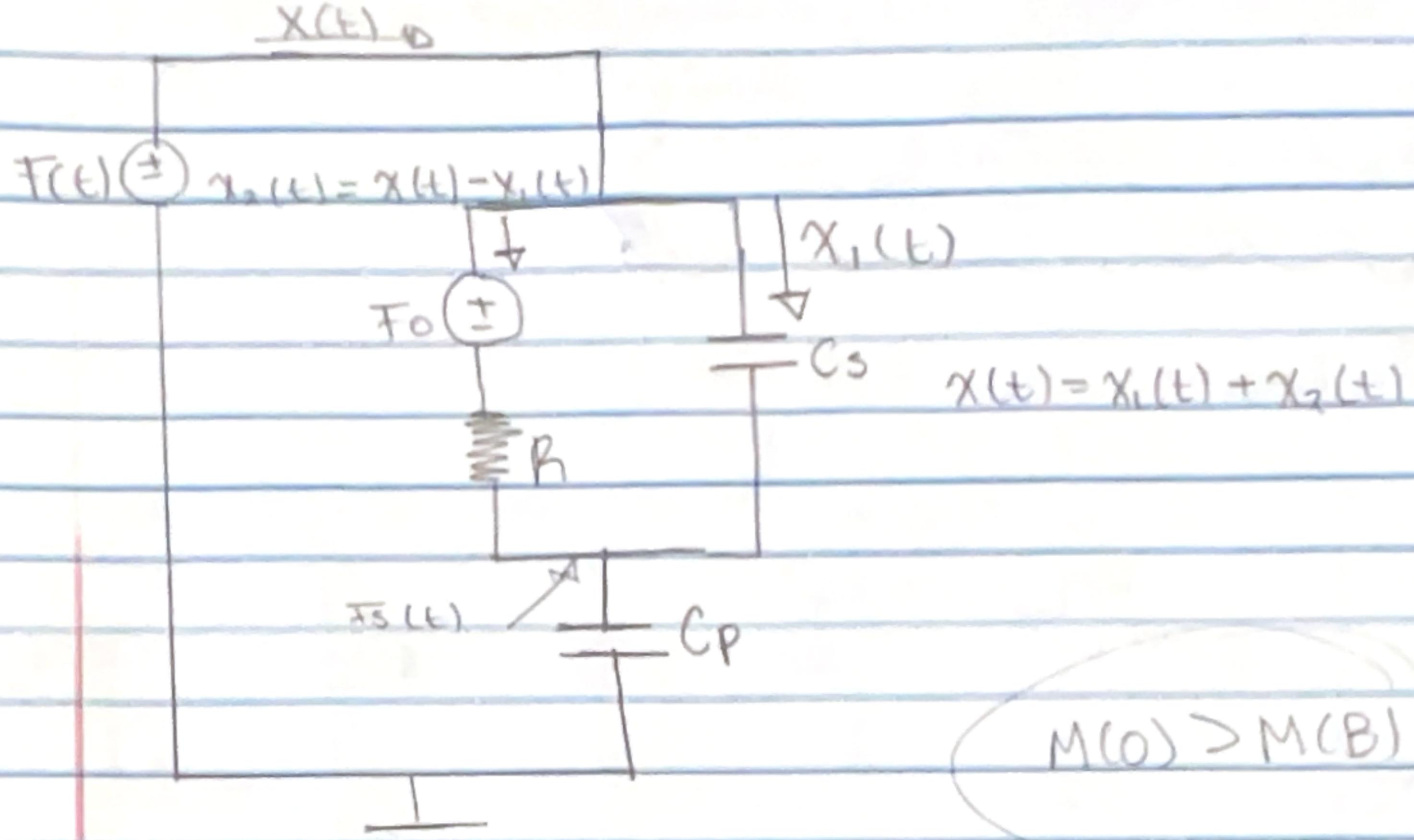


## Circuito eléctrico



## Función de transferencia

Análisis apagando  $F_0$

$$x(t) = x_1(t) + x_2(t)$$

$$x(t) = \frac{d[F_S(t)]}{dt} C_p$$

$$F(t) \quad x_2(t)$$

$$R$$

$$x_1(t)$$

$$C_s$$

$$x_2(t) = \frac{F(t) - F_S(t)}{R}$$

$$x_1(t) = C_s \frac{d[F(t) - F_S(t)]}{dt}$$

$$C_p = \frac{dF_S(t)}{dt} = C_s \frac{d(F(t) - F_S(t))}{dt} + \frac{F(t) - F_S(t)}{R}$$

$$C_p S F_S(s) = C_s S [F(s) - F_S(s)] + \frac{F(s) - F_S(s)}{R}$$


$$(C_p S + C_s S + \frac{1}{R}) F_S(s) = (C_s S + \frac{1}{R}) F(s)$$

$$\frac{F_S(s)}{F(s)} = \frac{(C_s S + \frac{1}{R})}{(C_p S + C_s S + \frac{1}{R})} = \frac{C_s S + \frac{1}{R}}{(C_p + C_s) S + \frac{1}{R}}$$

$$\frac{F_S(S)}{F(S)} = \frac{C_S R S + 1}{C_P R S + C_S R S + 1} = \frac{C_S R S + 1}{(C_P R + C_S R) S + 1}$$


$$F_{S_1}(S) = \frac{(C_S R S + 1) F(S)}{R((S + C_P) S + 1)}$$

\* Análisis apagando  $F(t)$

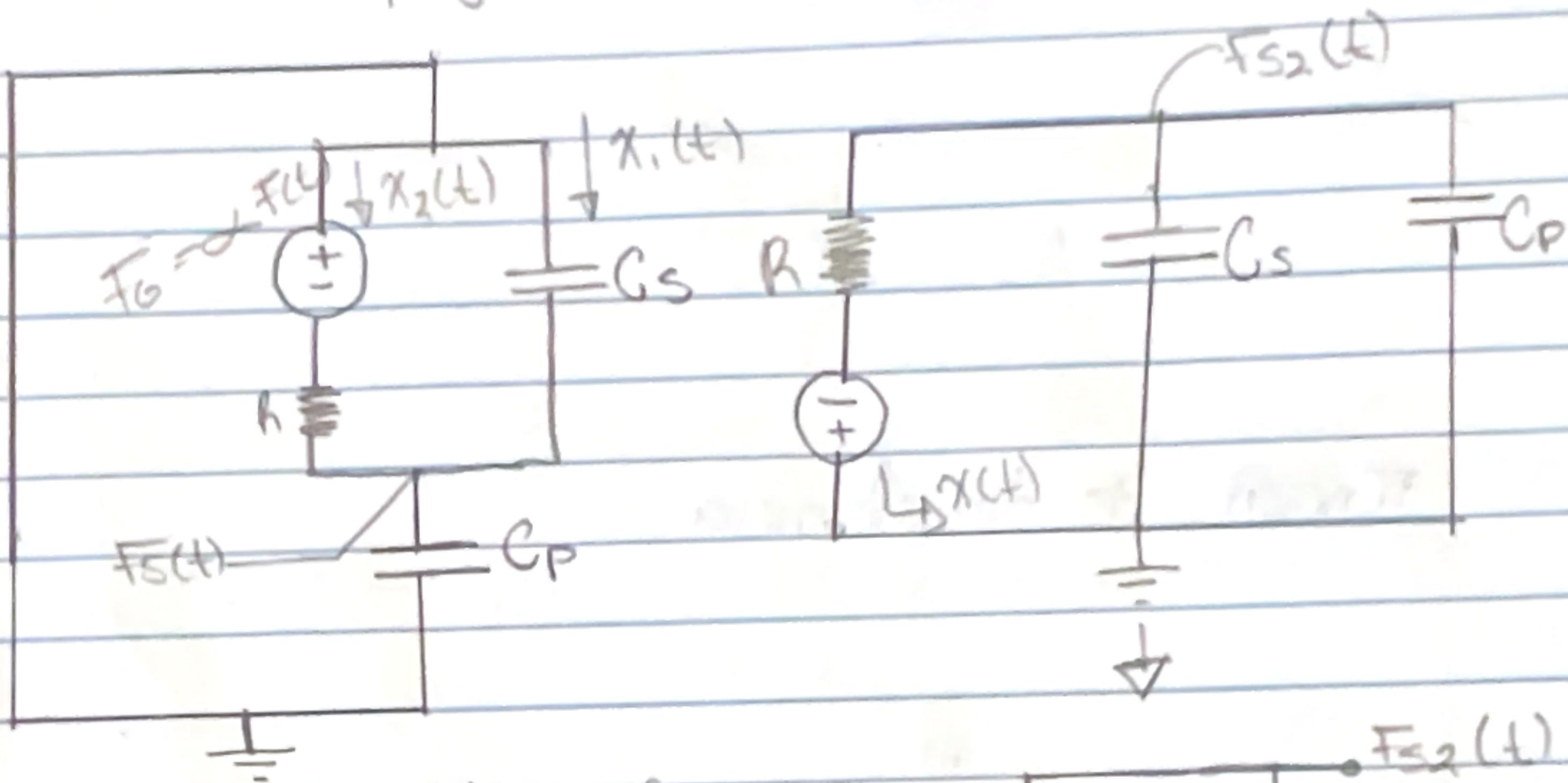

$$\alpha F(t) = R x(t) + \frac{1}{(S + C_P)} \int x(t) dt$$
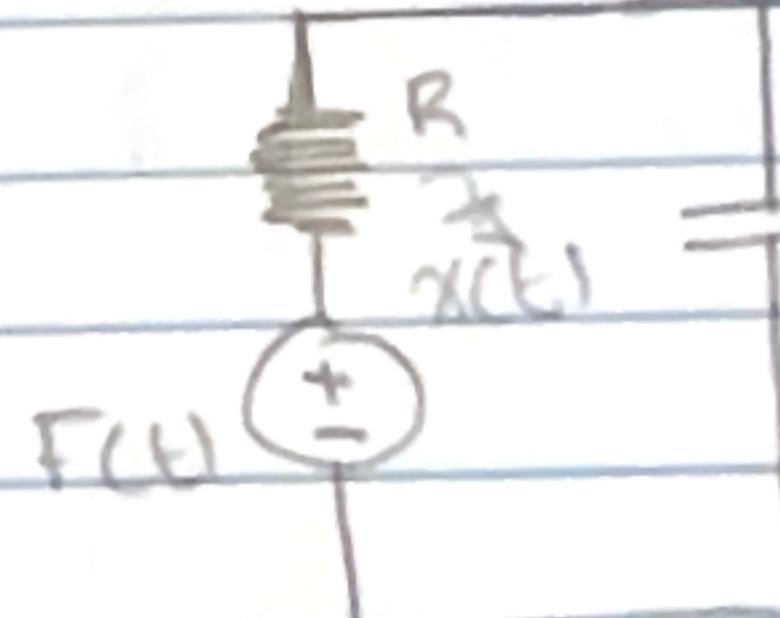
$$F_S(t) = \frac{1}{C_S + C_P} \int x(t) dt$$



Error de estado estacionario y lazo abierto

$$-\alpha F(S) = R x(S) + \frac{x(S)}{(S + C_P) S} = \frac{R x(S)}{-\alpha} - \frac{x(S)}{\alpha((S + C_P) S)}$$

$$F_S(S) = \frac{x(S)}{(S + C_P) S}$$

$$F_S = \frac{R x(S) (\cancel{(S + C_P) S}) + \cancel{\alpha x(S)}}{-\cancel{\alpha^2} ((S + C_P) S)}$$

$$= \frac{x(S) [R ((S + C_P) S + 1)]}{-\alpha ((S + C_P) S)}$$

$$\frac{F_S(S)}{F_S} = \frac{(S + C_P) S}{x(S) R ((S + C_P) S + 1)} = \frac{\alpha}{R ((S + C_P) S + 1)}$$

$$F_{S2}(s) = \frac{-\alpha F_S}{R((s+C_P)s+1)}$$

$$F_S(s) = F_{S1}(s) + F_{S2}(s)$$

$$F_S(s) = \frac{((sR(s+C_P))F(s) - \alpha F(s))}{R((C_P+s)s+1)}$$

$$F_S(s) = C_S R s + 1 - \alpha$$

$$F(s) = R((C_P+s)s+1)$$

Error de estado estacionario.

$$\begin{aligned} e(s) &= \lim_{s \rightarrow \infty} s \cdot F(s) \left[ 1 - \frac{F_S(s)}{F(s)} \right] \\ &= \lim_{s \rightarrow \infty} \left( s \cdot \frac{1}{s} \cdot \left( 1 - \frac{C_S R s + 1 - \alpha}{R((C_P+s)s+1)} \right) \right) = 1 - 1 + \alpha \end{aligned}$$

$$e(s) = +\alpha$$

Estabilidad en lazo abierto

$$R((C_P+s)s+1) = 0$$

$$R((C_P+s)s+1) = -1$$

$$s = -\frac{1}{R((C_P+s)s+1)}$$